

Hardware & Architecture HW #6 – 100 Pts

1. (8 Pts) For a $\overline{S} - \overline{R}$ Flip-Flop
 - a. Construct the basic un-clocked Logic Diagram for the circuit functionality
 - b. Draw the State Transition Diagram
 - c. Create the State Transition Table
 - d. Derive the characteristic (next-state) equation

2. (8 Pts) For a $S - R$ Flip-Flop
 - a. Construct the Logic Diagram for the circuit functionality
 - b. Draw the State Transition Diagram
 - c. Create the State Transition Table
 - d. Derive the characteristic (next-state) equation

3. (8 Pts) For a Negative-Edge Triggered $J - K$ Flip-Flop with Active-Low Preset and Clear
 - a. Draw the State Transition Diagram
 - b. Create the State Transition Table
 - c. Derive the characteristic (next state) equation
 - d. Draw the Block Diagram

Hardware & Architecture HW #6 – 100 Pts


4. (8 Pts) A Positive-Edge Triggered T Flip-Flop toggles the output when the T-Input is high
 - a. Draw the State Transition Diagram
 - b. Create the State Transition Table
 - c. Derive the characteristic (next state) equation
 - d. Draw the Block Diagram

5. (4 Pts) Create a T Flip-Flop using
 - a. J-K Flip Flop and basic logic gates, if needed
 - b. Using a D Flip Flop and basic logic gates, if needed

6. (2 Pt) Design a gated D-latch using only NAND gates and one inverter.

Hardware & Architecture HW #6 – 100 Pts

 7. (8 Pts) A latch can be constructed from an OR gate, an AND gate, and an Inverter as follows:



- What restriction must be placed on R and H so that P will always equal Q' (under steady-state conditions)?
 - Draw the State Transition Diagram
 - Construct the State Transition Table
 - Derive the characteristic (next state) equation
8. (16 Pts) A Reset-Dominant Flip-Flop behaves like an S-R Flip-Flop, except that the input $S=R=1$ is allowed and will cause the Latch to Reset
- Draw the State Transition Diagram
 - Construct the State Transition Table
 - Derive the characteristic (next state) equation
 - Show how a Reset-Dominant latch can be constructed by adding gate(s) to an S-R latch.
 - Repeat a – d for a Set-Dominant Flip-Flop, where $S=R=1$ is allowed and will Set the Latch.
9. (6 Pts) Design the following conversions by adding external gates
- D Flip-Flop to a J-K Flip-Flop
 - T Flip-Flop to a D Flip-Flop
 - T Flip-Flop to a D flip-Flop with Clock Enable

Hardware & Architecture HW #6 – 100 Pts

- 10.** (4 Pts) Design a 4-bit register with Data, Load, Clock, and Clear Inputs using D-Flip-Flops. Draw the circuit and explain the function of the design.
- 11.** (4 Pts) Design a Synchronous Serial-In / Serial-Out clocked 8-bit Shift Register using S-R Flip-Flops and an Inverter. Draw the circuit and explain the function of the design.
- 12.** (24 Pts) A stoplight is basically a 3-State Shift Register that shifts from the “Green” state to the “Yellow” state to the “Red”, and back to “Green” state based on a Transition input.
- a.** Derive the logic equation for the Transition Input.
 - b.** Is the equations for the Transition Input, combinatorial, sequential, or both. Explain
 - c.** Draw the State Transition Diagram for the Stoplight with the Transition Input
 - d.** Derive the State Transition Table for the Stoplight with the Transition Input
 - e.** Derive the characteristic (next state) equations for the Stoplight with the Transition Input